

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Low & High-frequency response of single-stage amplifier**

**Numerical 1:** For the circuit shown in figure 1, determine  $I_{CQ}$ , lower cut-off frequency due to  $C_S$ ,  $C_C$ ,  $C_E$ , overall cut-off frequency  $f_L$  and midband voltage in dB.  
 Given:  $\beta = 100$ ,  $r_o = \infty$

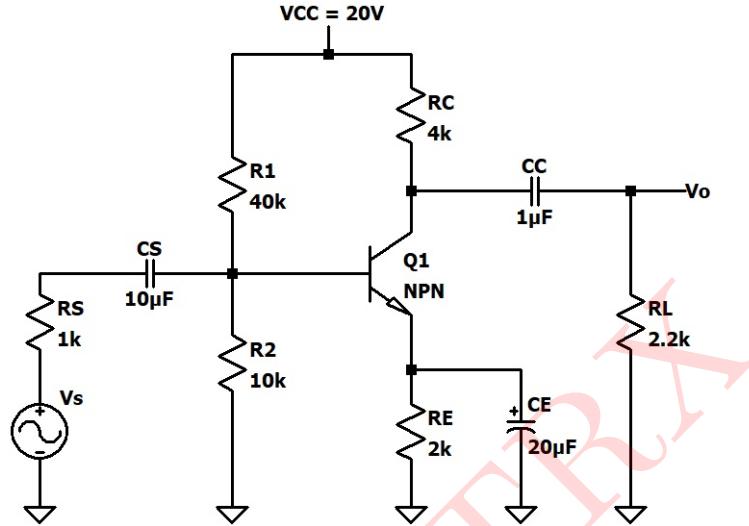


Figure 1: Circuit 1

**Solution:**

The given circuit 1 is a voltage divider bias configuration employing npn BJT. For DC biasing, the capacitors will act as an open source.

**DC Analysis:**

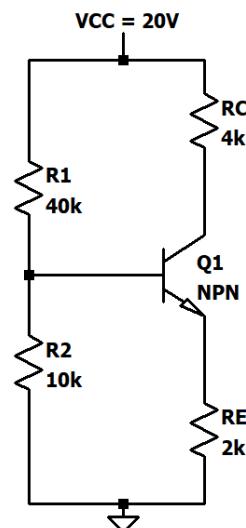


Figure 2: DC Equivalent Circuit

$$R_B = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_B = \frac{40 \times 10^3 \times 10 \times 10^3}{40 \times 10^3 + 10 \times 10^3} = 8 \text{ k}\Omega$$

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

$$V_G = \frac{20 \times 10 \times 10^3}{40 \times 10^3 + 10 \times 10^3} = 4 \text{ V}$$

Thevenin's Equivalent circuit:

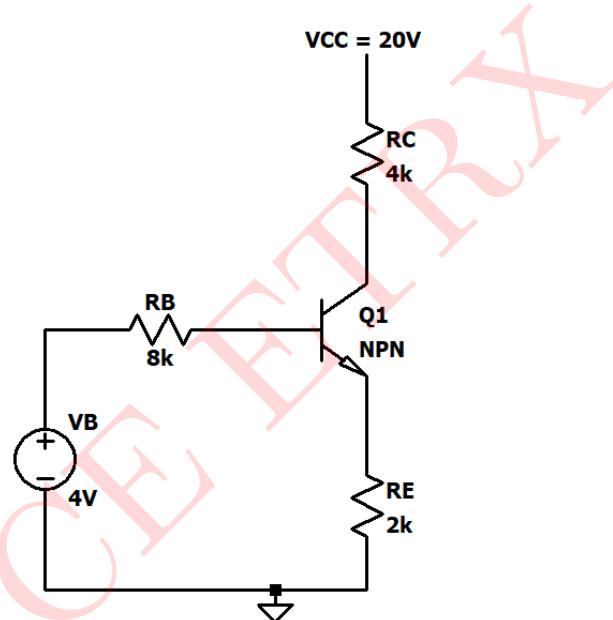


Figure 3: Thevenin's Equivalent circuit

$I_{BQ}$  can be calculated by applying KVL to the base-emitter loop,

$$V_B - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_B R_B + (1 + \beta) I_B R_E = V_B - V_{BE} \quad \dots (\because I_E = (1 + \beta) I_B)$$

$$I_B (R_B + (1 + \beta) R_E) = V_B - V_{BE}$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$I_B = \frac{4 - 0.7}{8 \times 10^3 + (1 + 100) \times 2 \times 10^3} = 15.71 \mu\text{A}$$

$$I_{CQ} = \beta I_B$$

$$I_{CQ} = 100 \times 15.71 \times 10^{-6} = 1.571 \text{ mA}$$

$$I_E = (1 + \beta) I_B$$

$$I_E = (1 + 100) \times 15.71 \times 10^{-6} = 1.586 \text{ mA}$$

### AC Analysis:

$$r_\pi = \frac{\beta V_T}{I_E}$$

$$r_\pi = \frac{10 \times 26 \times 10^{-3}}{1.586 \times 10^{-3}} = 1.64 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$g_m = \frac{1.571 \times 10^{-3}}{26 \times 10^{-3}} = 60.423 \text{ mA/V}$$

$$r_0 = \infty \quad \dots(\text{given})$$

Small Signal Equivalent Circuit is shown in figure 4:

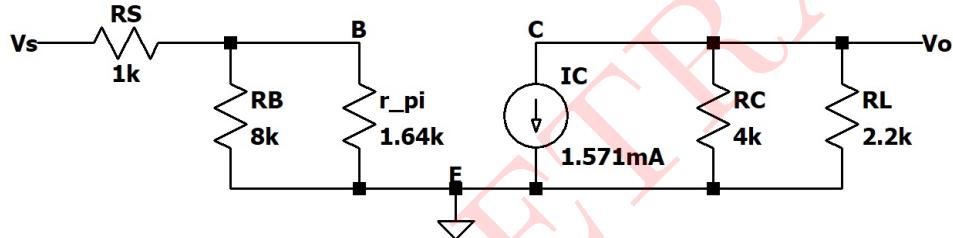


Figure 4: Small Signal Equivalent Circuit

\$V\_o\$ = voltage developed across \$(R\_c \parallel R\_L)\$

$$V_o = -g_m V_\pi (R_c \parallel R_L) \quad \dots(1)$$

but, \$V\_\pi\$ = voltage across \$(R\_B \parallel r\_\pi)\$

$$V_\pi = \frac{(R_B \parallel r_\pi)}{R_S + (R_B \parallel r_\pi)} V_s$$

Substituting this in equation 1,

$$V_o = -g_m \frac{(R_B \parallel r_\pi) V_s}{R_S + (R_B \parallel r_\pi)} (R_C \parallel R_L)$$

$$\frac{V_o}{V_s} = A_{V(mid)} = -g_m (R_C \parallel R_L) \frac{(R_B \parallel r_\pi)}{R_S + (R_B \parallel r_\pi)}$$

$$A_{V(mid)} = -60.423 \times 10^{-3} \frac{(4 \times 10^3 \parallel 2.2 \times 10^3) \times (8 \times 10^3 \parallel 1.64 \times 10^3)}{1 \times 10^3 + (8 \times 10^3 \parallel 1.64 \times 10^3)}$$

$$A_{V(mid)} = \frac{-60.423 \times 10^{-3} \times 1.419 \times 10^3 \times 1.361 \times 10^3}{1 \times 10^3 + 1.361 \times 10^3} = -49.425$$

$$A_{V(mid)dB} = 20 \log_{10}(|A_{V(mid)}|)$$

$$A_{V(mid)dB} = 20 \log_{10}(49.425) = 33.8789 \text{ dB}$$

Lower cut-off frequency analysis:

a) Due to  $C_S$  alone

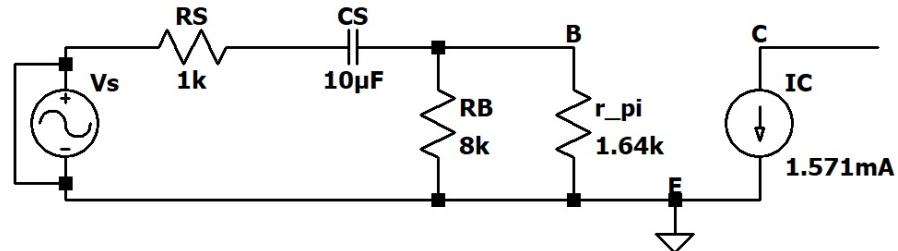


Figure 5: Small Signal Low Frequency Equivalent Circuit for  $C_S$  alone

$$R_i = R_B \parallel r_\pi$$

$$R_i = (8 \times 10^3 \parallel 1.64 \times 10^3) = 1.361 \text{ k}\Omega$$

$$f_{LC_S} = \frac{1}{2\pi C_S R_{eq}}$$

$$f_{LC_S} = \frac{1}{2\pi C_S (R_S + R_i)}$$

$$f_{LC_S} = \frac{1}{2\pi \times 10 \times 10^{-6} \times (1 \times 10^3 + 1.361 \times 10^3)} = 6.741 \text{ Hz}$$

b) Due to  $C_C$  alone

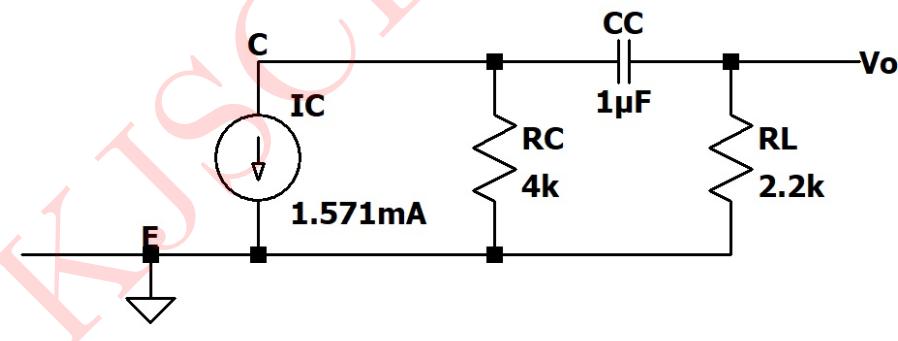


Figure 6: Small Signal Low Frequency Equivalent Circuit for  $C_C$  alone

$$R_{eq} = R_C + R_L$$

$$R_{eq} = 4 \times 10^3 + 2.2 \times 10^3 = 6.2 \text{ k}\Omega$$

$$f_{LC_C} = \frac{1}{2\pi C_C R_{eq}}$$

$$f_{LC_C} = \frac{1}{2\pi \times 1 \times 10^{-6} \times 6.2 \times 10^3} = 25.67 \text{ Hz}$$

b) Due to  $C_E$  alone

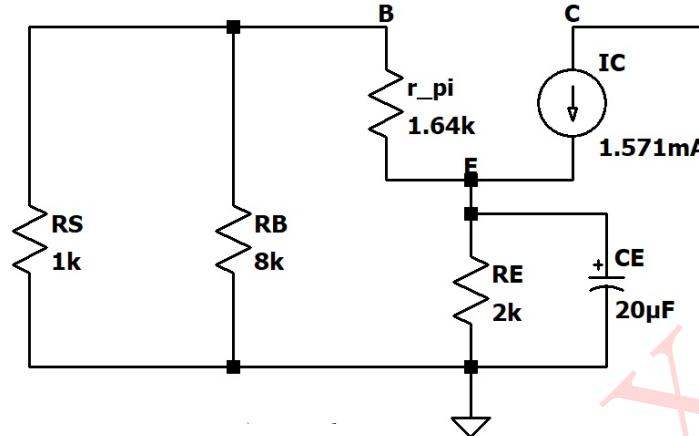


Figure 7: Small Signal Low Frequency Equivalent Circuit for  $C_E$  alone

$$R_{eq} = R_E \parallel \left( \frac{(R_S \parallel R_B) + r_\pi}{(1 + \beta)} \right)$$

$$R_{eq} = 2 \times 10^3 \parallel \left( \frac{(1 \times 10^3 \parallel 8 \times 10^3) + 1.64 \times 10^3}{1 + 100} \right) = 24.73 \Omega$$

$$f_{LC_E} = \frac{1}{2\pi C_C R_{eq}}$$

$$f_{LC_E} = \frac{1}{2\pi \times 20 \times 10^{-6} \times 24.73} = 321.785 \text{ Hz}$$

Overall cut-off frequency  $f_L$  will be the highest  $f_L$  among  $C_S$ ,  $C_C$  and  $C_E$

$f_L = f_{LC_E}$  ... ( $\because C_E$  has highest  $f_L$ )

$f_L = 321.785 \text{ Hz}$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

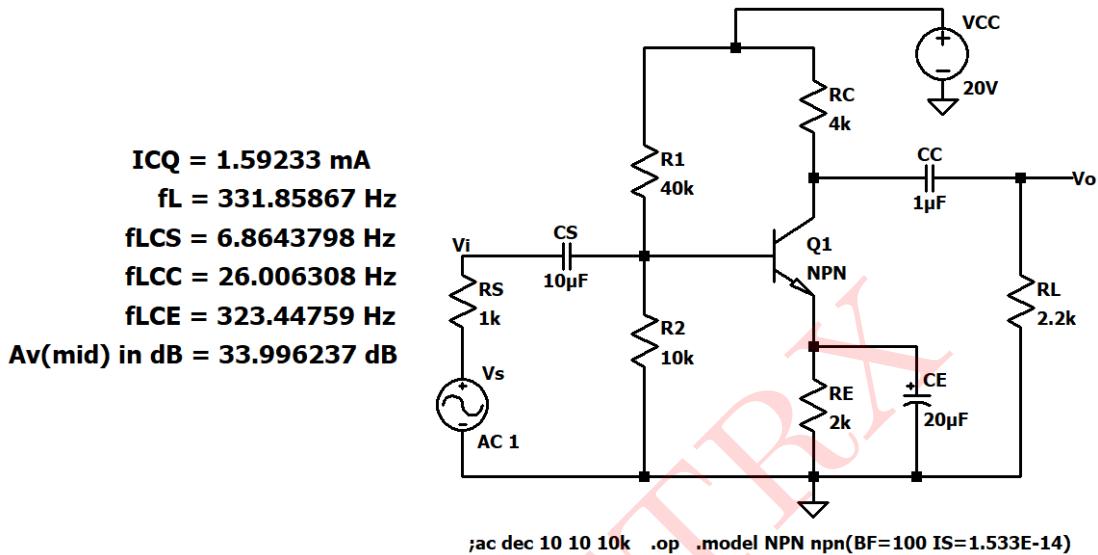


Figure 8: Circuit Schematic 1: Results


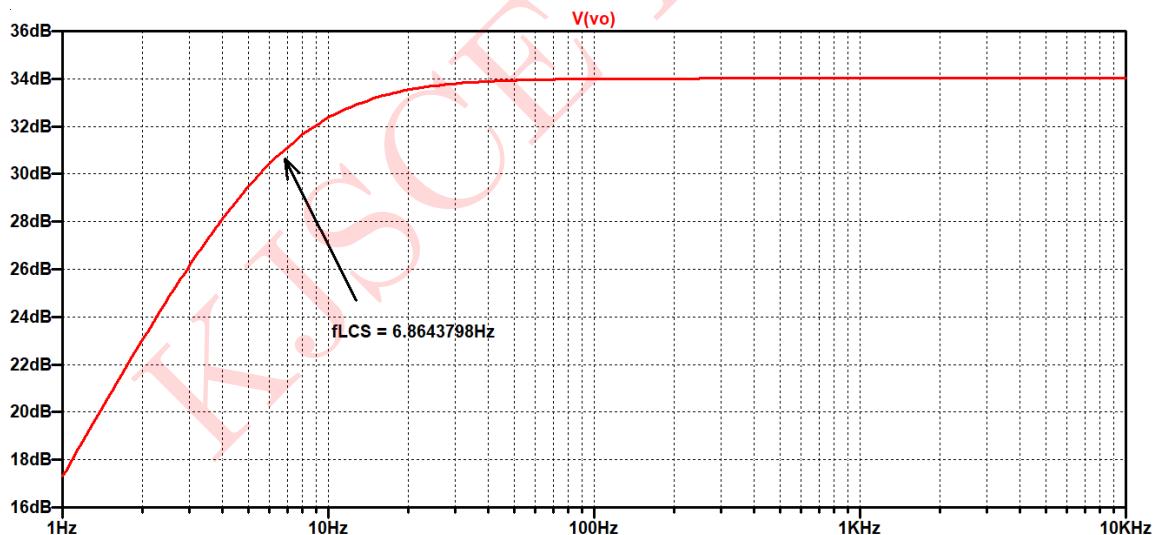
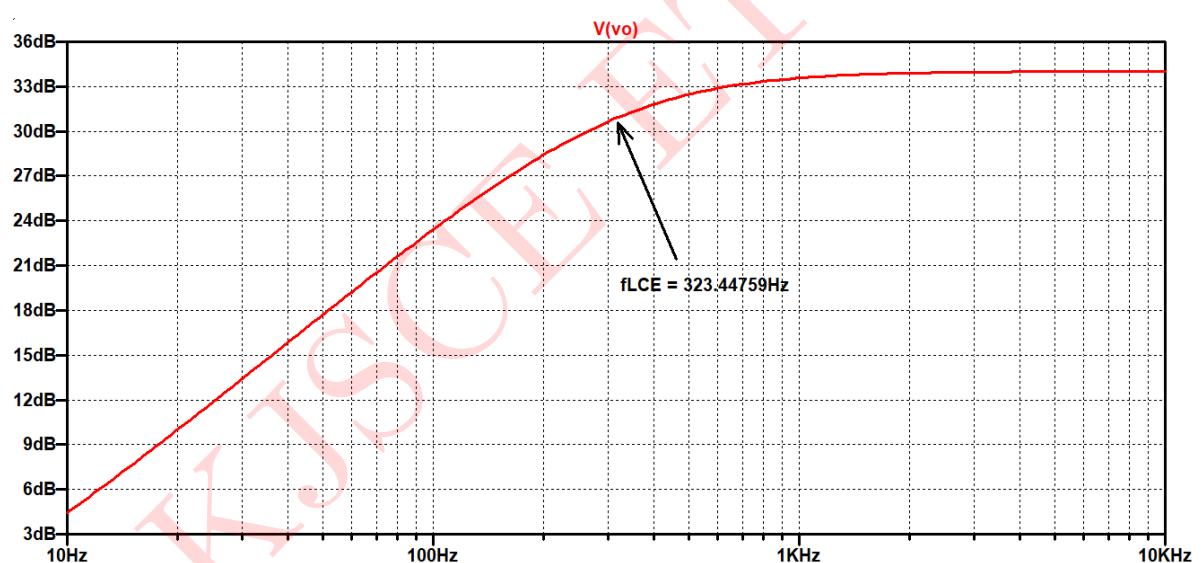


Figure 9: Low Frequency Response for  $C_S$  alone

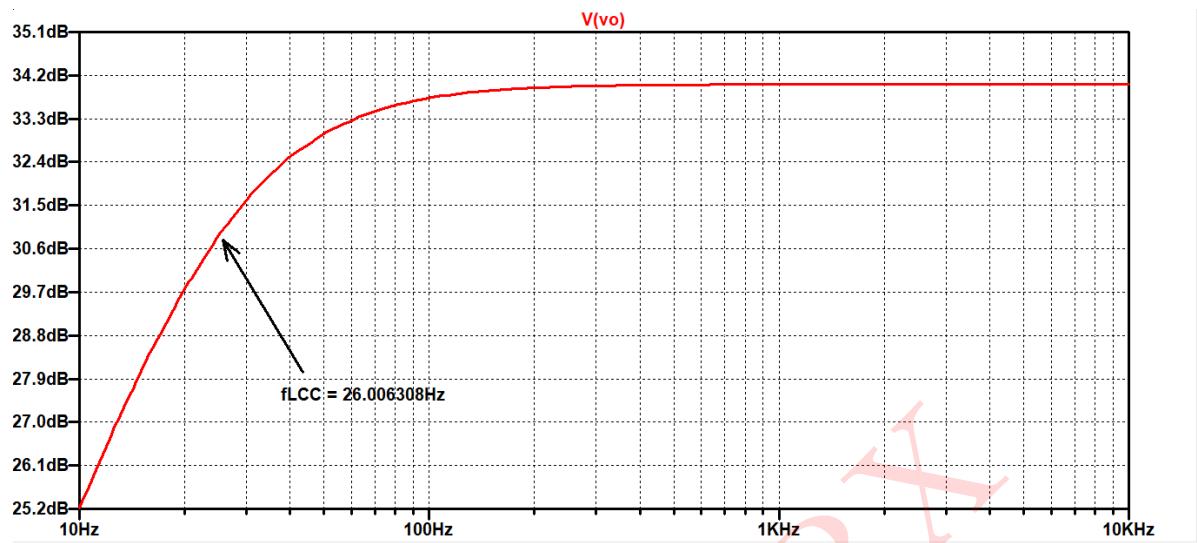

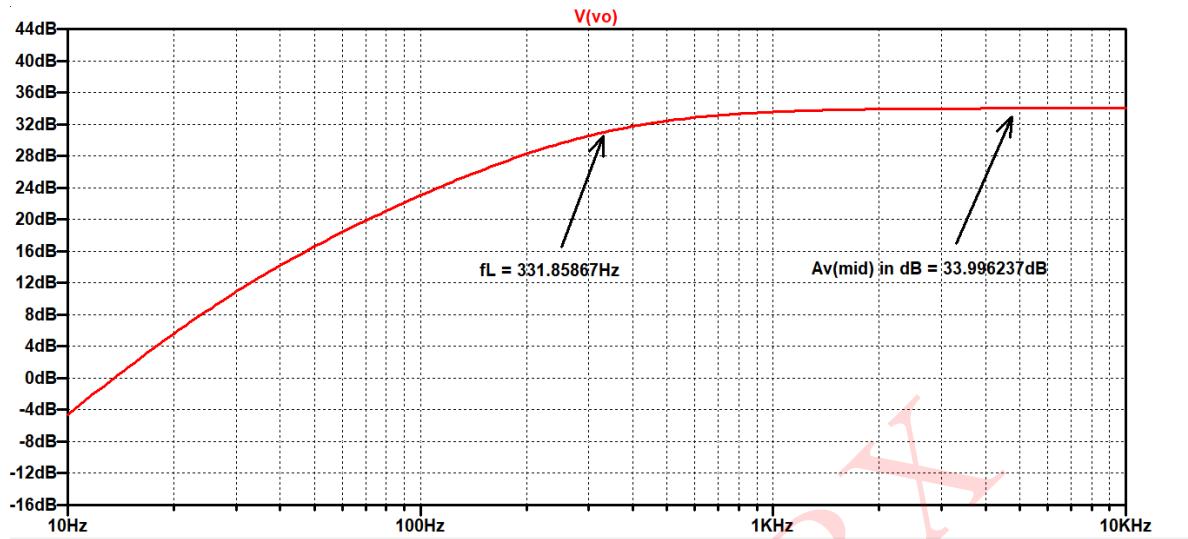


Figure 12: Low Frequency Response for the Circuit

**Comparison of theoretical and simulated values:**

Parameters	Theoretical Values	Simulated Values
$I_{CQ}$	1.571 mA	1.5923 mA
Lower cut-off frequency due to $C_S$	6.741 Hz	6.8643 Hz
Lower cut-off frequency due to $C_C$	25.67 Hz	26.0063 Hz
Lower cut-off frequency due to $C_E$	321.785 Hz	323.4475 Hz
Overall cut-off frequency $f_L$	321.785 Hz	331.8586 Hz
Midband voltage gain $A_{V(mid)}$ in dB	33.8789 dB	33.9962 dB

Table 1: Numerical 1

**Numerical 2:** For the circuit shown in figure 13, the transistor parameters are:  $k_n = 0.8 \text{ mA/V}^2$ ,  $V_{TN} = 2 \text{ V}$ ,  $\lambda = 0$ . Determine  $I_{DQ}$ ,  $V_{GSQ}$ , midband voltage gain in dB, lower cut-off frequency due to  $C_{C1}$ ,  $C_{C2}$ ,  $C_S$  and overall cut-off frequency  $f_L$

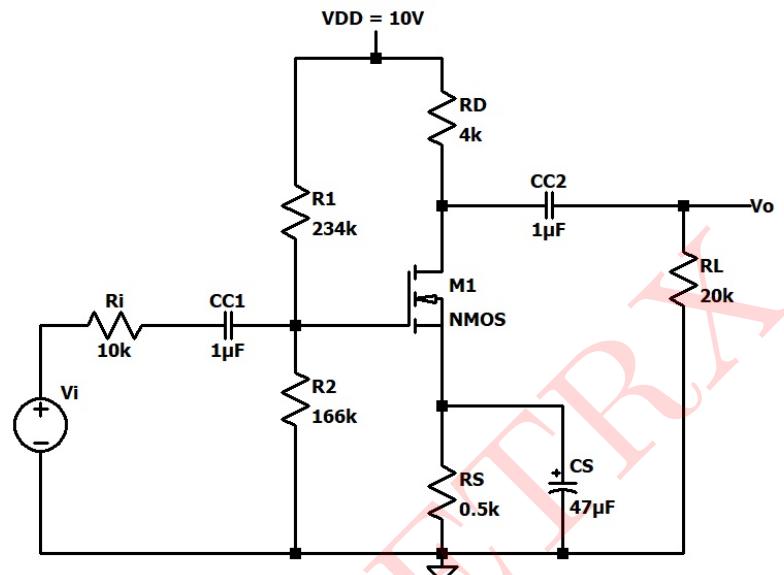


Figure 13: Circuit 2

### Solution:

The given circuit 2 is a voltage divider bias configuration employing NMOS. For DC biasing, the capacitors will act as an open source.

### DC Analysis:

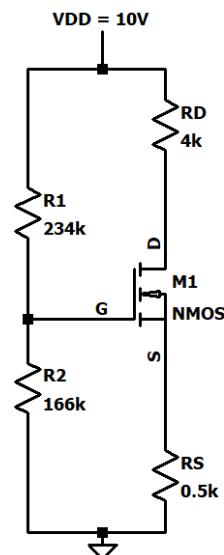


Figure 14: DC Equivalent Circuit

$$R_G = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_B = \frac{234 \times 10^3 \times 166 \times 10^3}{234 \times 10^3 + 166 \times 10^3} = 97.11 \text{ k}\Omega$$

$$V_G = \frac{V_{DD} \times R_2}{R_1 + R_2}$$

$$V_G = \frac{10 \times 166 \times 10^3}{234 \times 10^3 + 166 \times 10^3} = 4.15 \text{ V}$$

Thevenin's Equivalent circuit:

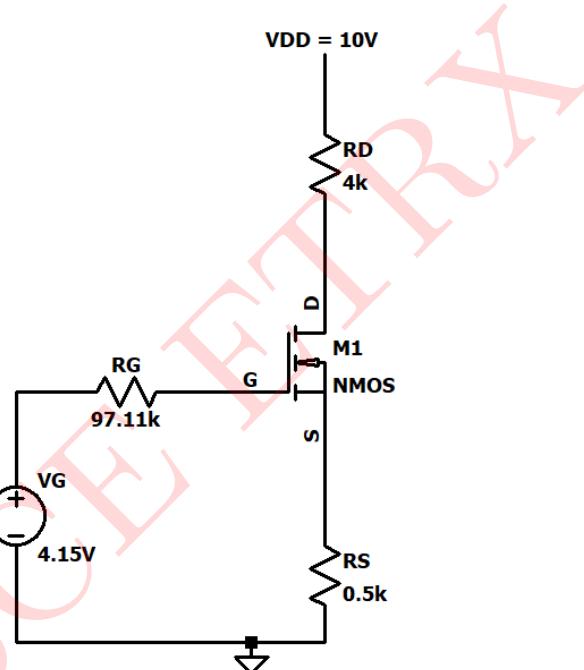


Figure 15: Thevenin's Equivalent circuit

$V_{GS}$  can be calculated by applying KVL to the gate-source loop,

$$V_G - I_G R_G - V_{GS} - I_D R_S = 0$$

$$V_{GS} = V_G - I_D R_S \quad \dots (\because I_G = 0)$$

$$V_{GS} = 4.15 - I_D 0.5 \times 10^3 \quad \dots (1)$$

From current equation,

$$I_D = k_n (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$I_D = k_n (V_{GS} - V_{TN})^2 \quad \dots (\because \lambda = 0)$$

$$I_D = 0.8 \times 10^{-3} (4.15 - 0.5 \times 10^3 I_D - 2)^2 \quad \dots (\text{from 1})$$

$$I_D = 0.8 \times 10^{-3} (2.15 - 0.5 \times 10^3 I_D)^2$$

$$I_D = 0.8 \times 10^{-3} (4.6225 - 2.15 \times 10^3 I_D + 0.25 \times 10^6 I_D^2)$$

$$I_D = 3.698 \times 10^{-3} - 1.72 I_D + 200 I_D^2$$

$$200 I_D^2 - 2.72 I_D + 3.698 \times 10^{-3} = 0$$

$$I_D = 12.06 \text{ mA or } I_D = 1.53 \text{ mA}$$

Let,  $I_D = 12.06 \text{ mA}$

$$V_{GS} = 4.15 - 12.06 \times 10^{-3} \times 0.5 \times 10^3 = -1.88 \text{ V}$$

Let,  $I_D = 1.53 \text{ mA}$

$$V_{GS} = 4.15 - 1.53 \times 10^{-3} \times 0.5 \times 10^3 = 3.385 \text{ V}$$

$V_{GS}$  cannot be negative for n-mosfet.

$$I_{DQ} = 1.53 \text{ mA}$$

$$V_{GSQ} = 3.385 \text{ V}$$

### AC Analysis:

$$g_m = 2k_n(V_{GS} - V_{TN})$$

$$g_m = 2 \times 0.8 \times 10^{-3}(3.385 - 2) = 2.216 \text{ mA/V}$$

$$r_d = \frac{1}{\lambda I_{DQ}} = \frac{1}{0} = \infty \quad \dots(\text{given})$$

Small Signal Equivalent Circuit is shown in figure 16:

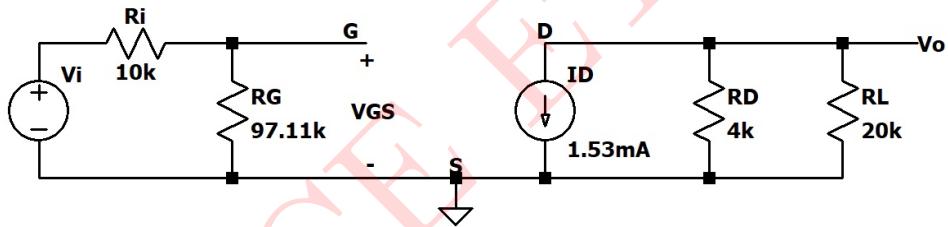


Figure 16: Small Signal Equivalent Circuit

Output voltage  $V_o$  = voltage developed across  $(R_D \parallel R_L)$  due to  $g_m V_{gs}$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$V_{gs} = \frac{R_G}{R_G + R_i} V_i \quad \dots(\text{Voltage divider})$$

$$V_o = -g_m \left( \frac{R_G}{R_G + R_i} \right) V_i (R_D \parallel R_L)$$

$$\frac{V_o}{V_i} = A_{V(mid)} = -g_m \left( \frac{R_G}{R_G + R_i} \right) (R_D \parallel R_L)$$

$$A_{V(mid)} = -2.216 \times 10^{-3} \left( \frac{97.11 \times 10^3}{97.11 \times 10^3 + 10 \times 10^3} \right) (4 \times 10^3 \parallel 20 \times 10^3)$$

$$A_{V(mid)} = -2.216 \times 10^{-3} (0.9066) (3.33 \times 10^3) = -6.69$$

$$A_{V(mid)dB} = 20 \log_{10}(|A_{V(mid)}|)$$

$$A_{V(mid)dB} = 20 \log_{10}(6.69) = 16.5085 \text{ dB}$$

Lower cut-off frequency analysis:

a) Due to  $C_{C1}$  alone

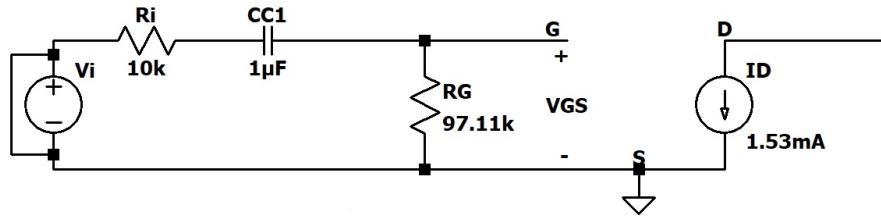


Figure 17: Small Signal Low Frequency Equivalent Circuit for  $C_{C1}$

$$R_{eq} = R_i + R_G$$

$$R_i = (10 \times 10^3 + 97.11 \times 10^3) = 107.11 \text{ k}\Omega$$

$$f_{LC_{C1}} = \frac{1}{2\pi C_{C1} R_{eq}}$$

$$f_{LC_S} = \frac{1}{2\pi \times 1 \times 10^{-6} \times 107.11 \times 10^3} = 1.4859 \text{ Hz}$$

b) Due to  $C_{C2}$  alone

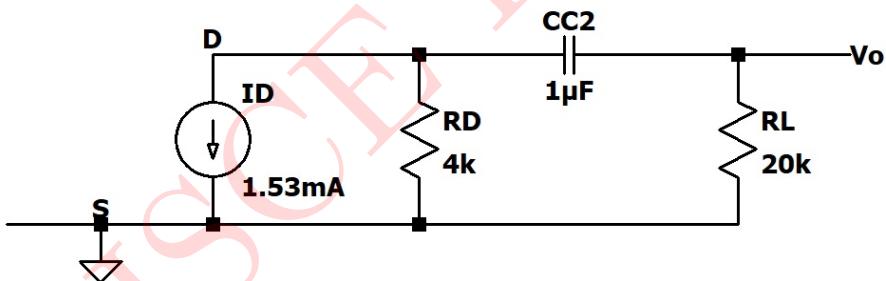


Figure 18: Small Signal Low Frequency Equivalent Circuit for  $C_{C2}$

$$R_{eq} = R_D + R_L$$

$$R_i = 4 \times 10^3 + 20 \times 10^3 = 24 \text{ k}\Omega$$

$$f_{LC_{C2}} = \frac{1}{2\pi C_{C2} R_{eq}}$$

$$f_{LC_S} = \frac{1}{2\pi \times 1 \times 10^{-6} \times 24 \times 10^3} = 6.6314 \text{ Hz}$$

b) Due to  $C_S$  alone

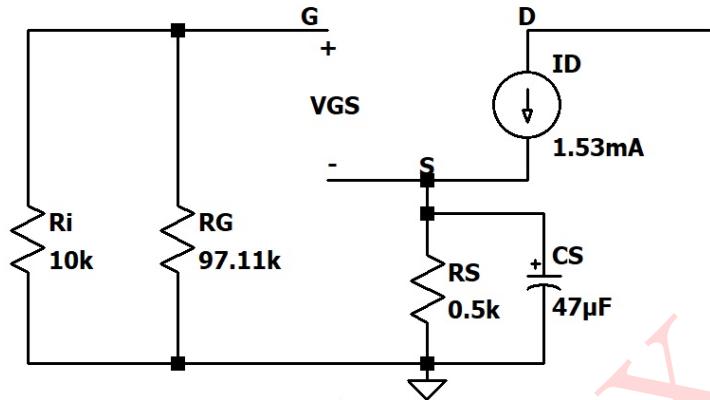


Figure 19: Small Signal Low Frequency Equivalent Circuit for  $C_S$

$$R_{eq} = R_S \parallel \left( \frac{1}{g_m} \right)$$

$$R_{eq} = 0.5 \times 10^3 \parallel \left( \frac{1}{2.216 \times 10^{-3}} \right) = 237.1916 \Omega$$

$$f_{LC_S} = \frac{1}{2\pi C_S R_{eq}}$$

$$f_{LC_S} = \frac{1}{2\pi \times 47 \times 10^{-6} \times 237.1916} = 14.2765 \text{ Hz}$$

Overall cut-off frequency  $f_L$  will be the highest  $f_L$  among  $C_{C1}$ ,  $C_{C2}$  and  $C_S$

$f_L = f_{LC_S}$  ...( $\because C_S$  has highest  $f_L$ )

$$f_L = 14.2765 \text{ Hz}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

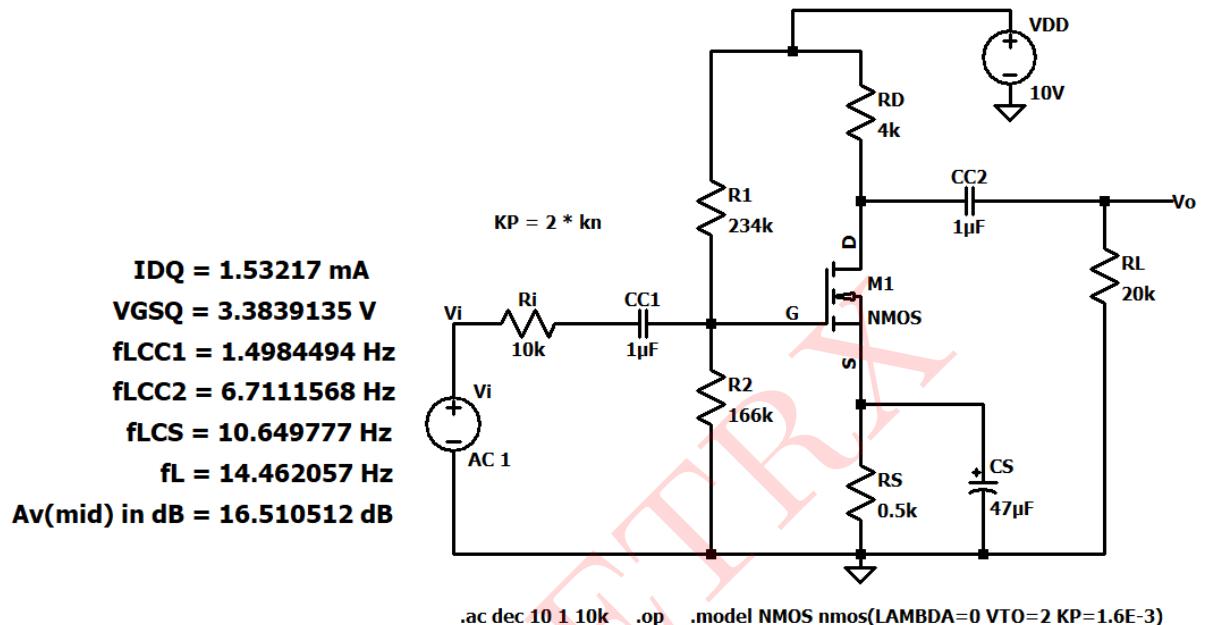


Figure 20: Circuit Schematic 2: Results

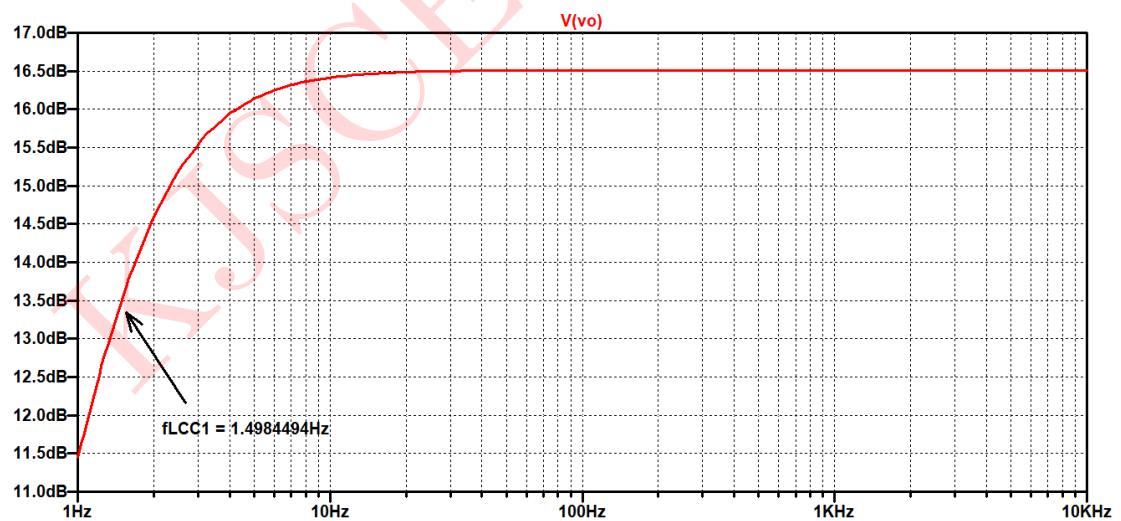


Figure 21: Low Frequency Response for  $C_{C1}$

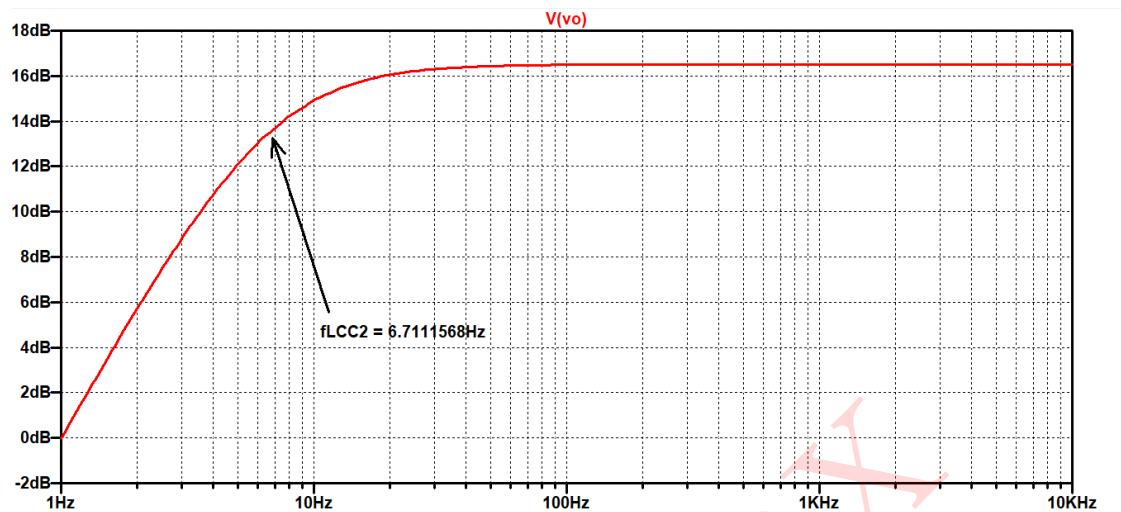


Figure 22: Low Frequency Response for  $C_{C2}$

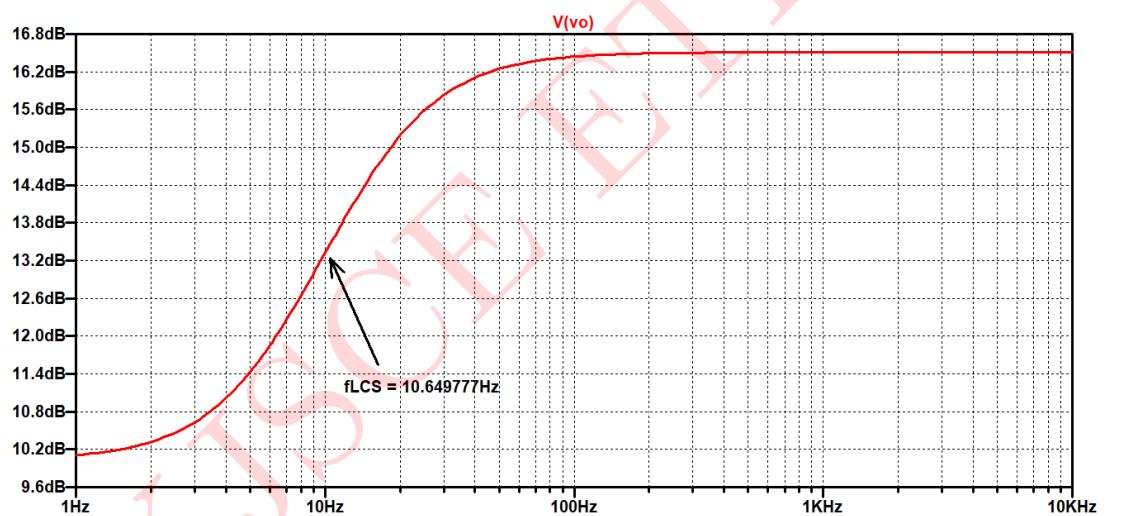


Figure 23: Low Frequency Response for  $C_S$

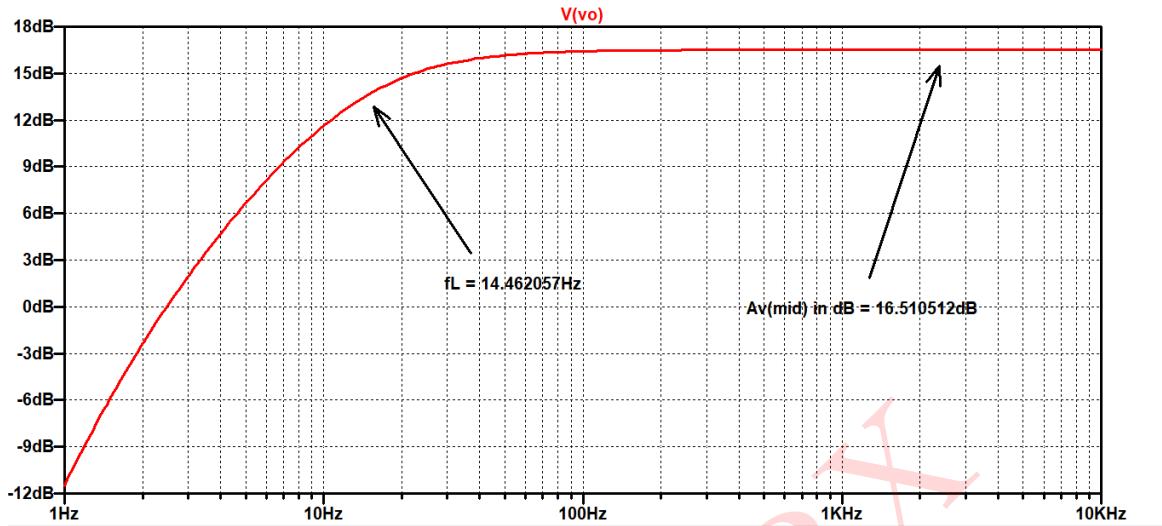


Figure 24: Low Frequency Response for the Circuit

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{DQ}$	1.53 mA	1.5321 mA
$V_{GSQ}$	3.385 V	3.3839 V
Lower cut-off frequency due to $C_{C1}$	1.4859 Hz	1.4984 Hz
Lower cut-off frequency due to $C_{C2}$	6.6314 Hz	6.7111 Hz
Lower cut-off frequency due to $C_S$	14.2765 Hz	10.6497 Hz
Overall cut-off frequency $f_L$	14.2765 Hz	14.4620 Hz
Midband voltage gain $A_V(mid)$ in dB	16.5085 dB	16.5105 dB

Table 2: Numerical 2

**Numerical 3:** For the circuit shown in figure 25, determine:  $I_{CQ}$ ,  $V_{CEQ}$ , lower cut-off frequency due to  $C_S$ ,  $C_C$  and  $C_E$ , overall cut-off frequency  $f_L$ , overall cut-off frequency  $f_H$  and midband voltage gain in dB.

Given:  $\beta = 100$ ,  $r_o = \infty$ ,  $C_{be} = 36 \text{ pF}$ ,  $C_{bc} = 4 \text{ pF}$ ,  $C_{ce} = 1 \text{ pF}$ ,  $C_{wi} = 6 \text{ pF}$ ,  $C_{wo} = 8 \text{ pF}$

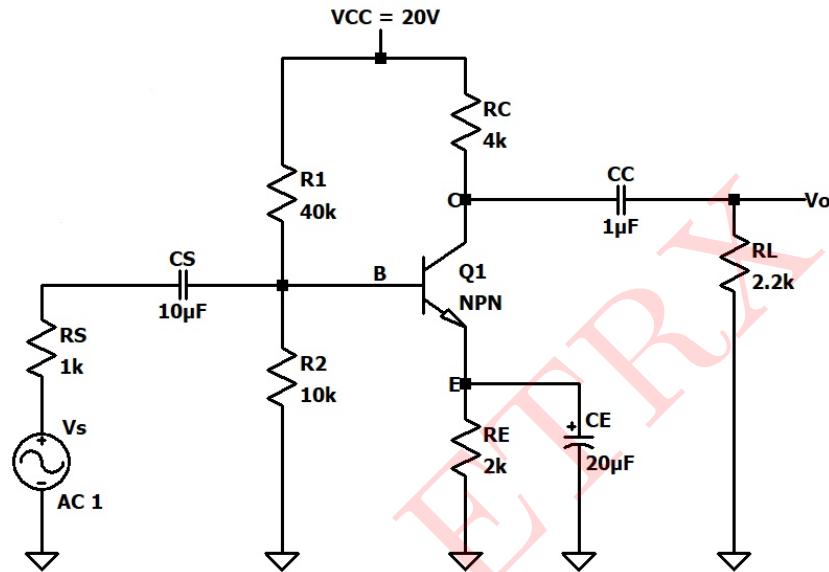


Figure 25: Circuit 3

### Solution:

The given circuit 3 is a voltage divider bias configuration employing npn BJT.

For DC biasing, the capacitors will act as an open source.

### DC Analysis:

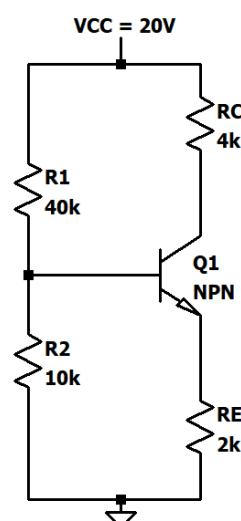


Figure 26: DC Equivalent Circuit

$$R_B = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_B = \frac{40 \times 10^3 \times 10 \times 10^3}{40 \times 10^3 + 10 \times 10^3} = 8 \text{ k}\Omega$$

$$V_G = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

$$V_G = \frac{20 \times 10 \times 10^3}{40 \times 10^3 + 10 \times 10^3} = 4 \text{ V}$$

Thevenin's Equivalent circuit:

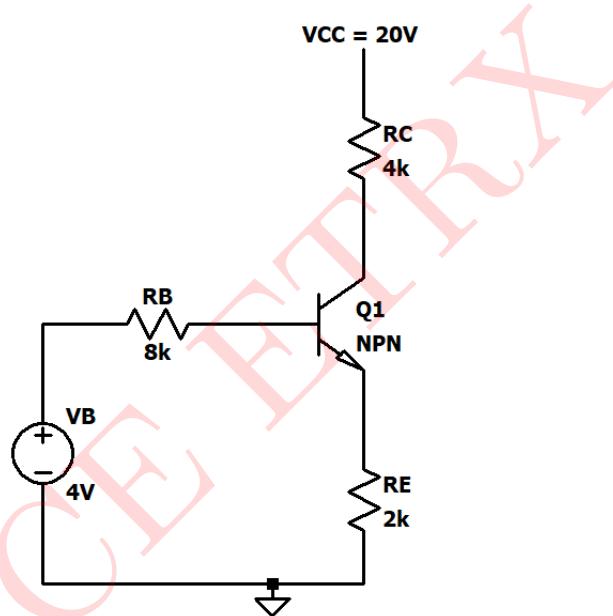


Figure 27: Thevenin's Equivalent circuit

$I_{BQ}$  can be calculated by applying KVL to the base-emitter loop,

$$V_B - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_B R_B + (1 + \beta) I_B R_E = V_B - V_{BE} \quad \dots (\because I_E = (1 + \beta) I_B)$$

$$I_B (R_B + (1 + \beta) R_E) = V_B - V_{BE}$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$I_B = \frac{4 - 0.7}{8 \times 10^3 + (1 + 100) \times 2 \times 10^3} = 15.71 \mu\text{A}$$

$$I_{CQ} = \beta I_B$$

$$I_{CQ} = 100 \times 15.71 \times 10^{-6} = 1.571 \text{ mA}$$

$$I_E = (1 + \beta) I_B$$

$$I_E = (1 + 100) \times 15.71 \times 10^{-6} = 1.586 \text{ mA}$$

$V_{CEQ}$  can be calculated by applying KVL to the collector-emitter loop,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$V_{CE} = 20 - 1.571 \times 10^{-3} \times 4 \times 10^3 - 1.586 \times 10^{-3} \times 2 \times 10^3 = \mathbf{10.544 \text{ V}}$$

### AC Analysis:

$$r_\pi = \frac{\beta V_T}{I_E}$$

$$r_\pi = \frac{100 \times 26 \times 10^{-3}}{1.586 \times 10^{-3}} = \mathbf{1.64 \text{ k}\Omega}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$g_m = \frac{1.571 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{60.423 \text{ mA/V}}$$

$$r_0 = \infty \quad \dots(\text{given})$$

Small Signal Equivalent Circuit is shown in figure 28:

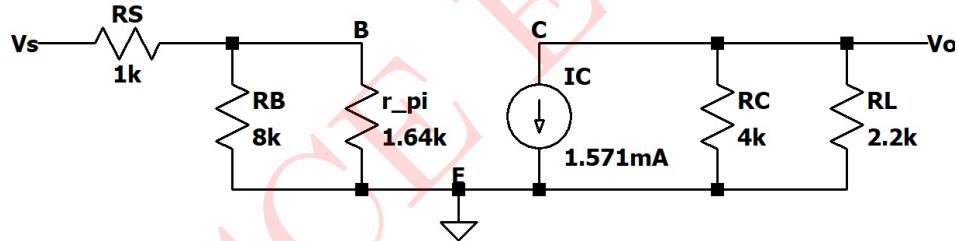


Figure 28: Small Signal Equivalent Circuit

Output voltage  $V_o$  = voltage developed across  $(R_C \parallel R_L)$  due to  $g_m V_\pi$

$$V_o = -g_m V_\pi (R_C \parallel R_L) \quad \dots(1)$$

$V_\pi$  = Voltage across  $(R_B \parallel r_\pi)$

$$V_\pi = \frac{(R_B \parallel r_\pi)}{R_S + (R_B \parallel r_\pi)} V_S \quad \dots(\text{Voltage divider})$$

Substituting in equation 1,

$$V_o = -g_m \frac{(R_B \parallel r_\pi)}{R_S + (R_B \parallel r_\pi)} V_S (R_C \parallel R_L)$$

$$\frac{V_o}{V_i} = A_{V(mid)} = -g_m (R_C \parallel R_L) \frac{(R_B \parallel r_\pi)}{R_S + (R_B \parallel r_\pi)}$$

$$A_{V(mid)} = -60.423 \times 10^{-3} \frac{(4 \times 10^3 \parallel 2.2 \times 10^3)(8 \times 10^3 \parallel 1.64 \times 10^3)}{1 \times 10^3 + (8 \times 10^3 \parallel 1.64 \times 10^3)}$$

$$A_{V(mid)} = \frac{-60.423 \times 10^{-3} \times 1.419 \times 10^3 \times 1.361 \times 10^3}{1 \times 10^3 + 1.361 \times 10^3} = \mathbf{-49.425}$$

$$A_{V(mid)dB} = 20 \log(|A_{V(mid)}|)$$

$$A_{V(mid)dB} = 20 \log(49.425) = \mathbf{33.8789 \text{ dB}}$$

Lower cut-off frequency analysis:

a) Due to  $C_S$  alone

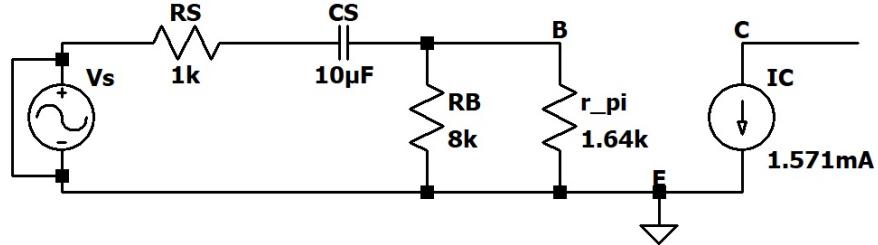


Figure 29: Small Signal Low Frequency Equivalent Circuit for  $C_S$  alone

$$R_i = R_B \parallel r_\pi$$

$$R_{eq} = 8 \times 10^3 \parallel 1.64 \times 10^3 = 1.361 \text{ k}\Omega$$

$$f_{LC_S} = \frac{1}{2\pi C_S R_{eq}}$$

$$f_{LC_S} = \frac{1}{2\pi C_S (R_S + R_i)}$$

$$f_{LC_S} = \frac{1}{2\pi \times 10 \times 10^{-6} \times (1 \times 10^3 + 1.361 \times 10^3)} = 6.741 \text{ Hz}$$

b) Due to  $C_C$  alone

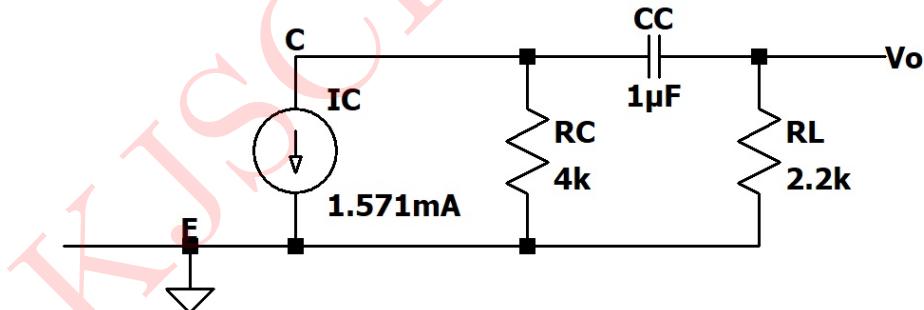


Figure 30: Small Signal Low Frequency Equivalent Circuit for  $C_C$  alone

$$R_{eq} = R_C + R_L$$

$$R_i = 4 \times 10^3 + 2.2 \times 10^3 = 6.2 \text{ k}\Omega$$

$$f_{LC_C} = \frac{1}{2\pi C_C R_{eq}}$$

$$f_{LC_C} = \frac{1}{2\pi \times 1 \times 10^{-6} \times 6.2 \times 10^3} = 25.67 \text{ Hz}$$

b) Due to  $C_E$  alone

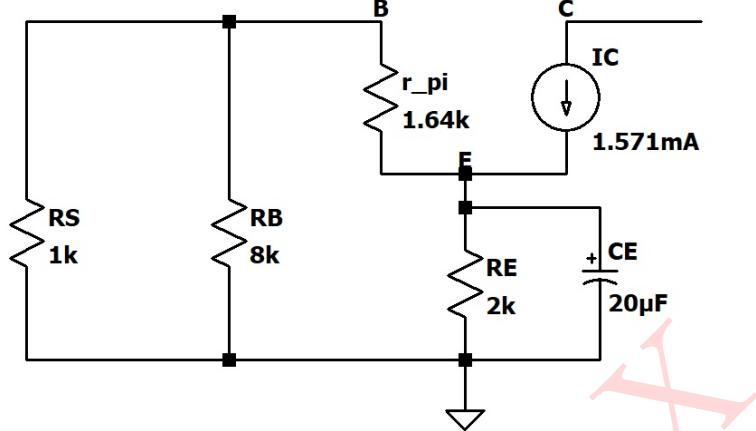


Figure 31: Small Signal Low Frequency Equivalent Circuit for  $C_E$  alone

$$R_{eq} = R_E \parallel \left( \frac{(R_S \parallel R_B) + r_\pi}{(1 + \beta)} \right)$$

$$R_{eq} = 2 \times 10^3 \parallel \left( \frac{(1 \times 10^3 \parallel 8 \times 10^3) + 1.64 \times 10^3}{1 + 100} \right) = 24.73 \Omega$$

$$f_{LC_E} = \frac{1}{2\pi C_E R_{eq}}$$

$$f_{LC_E} = \frac{1}{2\pi \times 20 \times 10^{-6} \times 24.73} = 321.785 \text{ Hz}$$

Overall cut-off frequency  $f_L$  will be the highest  $f_L$  among  $C_S$ ,  $C_C$  and  $C_E$

$$f_L = f_{LC_E} \quad \dots (\because C_E \text{ has highest } f_L)$$

$$f_L = 321.785 \text{ Hz}$$

Higher cut-off frequency analysis:

$$C_{mi} = (1 - A)C_\mu$$

$$C_{mi} = (1 - A)C_{bc} \quad \dots (\because C_\mu = C_{bc})$$

$$C_{mi} = (1 + 49.425) \times 4 \times 10^{-12} = 2.017 \times 10^{-10} \text{ F}$$

$$C_{mo} = \left( 1 - \frac{1}{A} \right) C_\mu$$

$$C_{mo} = \left( 1 - \frac{1}{A} \right) C_{bc} \quad \dots (\because C_\mu = C_{bc})$$

$$C_{mo} = \left( 1 - \frac{1}{-49.425} \right) \times 4 \times 10^{-12} = 4.08 \times 10^{-12} \text{ F}$$

$$C_i = C_{wi} + C_{be} + C_{mi}$$

$$C_i = 6 \times 10^{-12} + 36 \times 10^{-12} + 2.017 \times 10^{-10} = 2.247 \times 10^{-10} \text{ F}$$

$$C_o = C_{wo} + C_{ce} + C_{mo}$$

$$C_i = 8 \times 10^{-12} + 1 \times 10^{-12} + 4.08 \times 10^{-12} = 1.308 \times 10^{-11} \text{ F}$$

a) Due to  $C_i$  alone

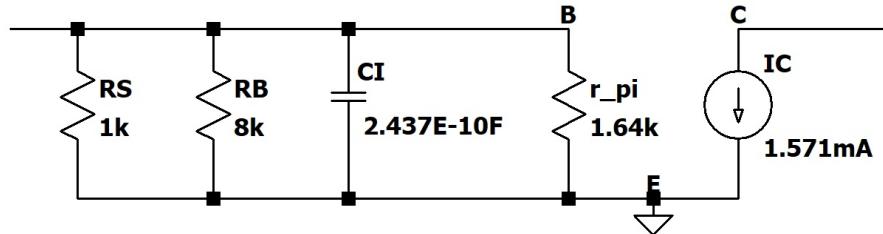


Figure 32: Small Signal High Frequency Equivalent Circuit for  $C_i$  alone

$$R_{eq} = R_S \parallel R_B \parallel r_\pi$$

$$R_{eq} = R_{eq} = 1 \times 10^3 \parallel 8 \times 10^3 \parallel 1.64 \times 10^3 = 576.45 \Omega$$

$$f_{Hi} = \frac{1}{2\pi C_i R_{eq}}$$

$$f_{Hi} = \frac{1}{2\pi \times 2.437 \times 10^{-10} \times 576.45} = 1.1329 \text{ MHz}$$

b) Due to  $C_o$  alone

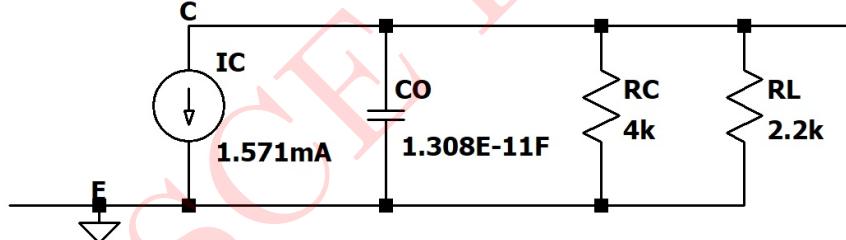


Figure 33: Small Signal High Frequency Equivalent Circuit for  $C_o$  alone

$$R_{eq} = R_C \parallel R_L$$

$$R_{eq} = 4 \times 10^3 \parallel 2.2 \times 10^3 = 1.419 \text{ k}\Omega$$

$$f_{Ho} = \frac{1}{2\pi C_o R_{eq}}$$

$$f_{Ho} = \frac{1}{2\pi \times 1.308 \times 10^{-11} \times 1.419 \times 10^3} = 8.5749 \text{ MHz}$$

Overall cut-off frequency  $f_H$  will be the lowest  $f_H$  among  $C_i$  and  $C_o$

$$f_H = f_{Hi} \quad \dots (\because C_i \text{ has highest } f_H)$$

$$f_H = 1.1329 \text{ MHz}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

**ICQ = 1.59233 mA**  
**VCEQ = 10.414156 V**  
**fL = 332.95693Hz**  
**fH = 1.2011631 MHz**  
**fLCS = 6.8643798 Hz**  
**fLCC = 26.006308 Hz**  
**fLCE = 323.44759 Hz**  
**Av(mid) in dB = 34.013424 dB**

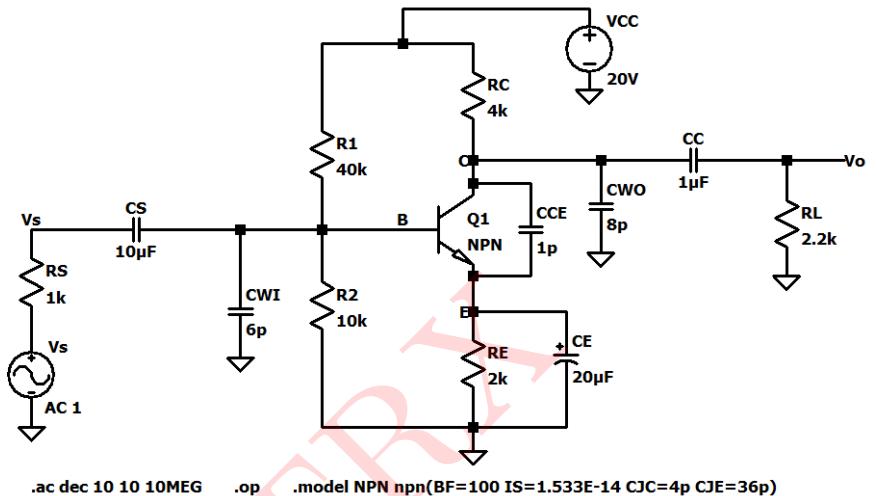


Figure 34: Circuit Schematic 3: Results

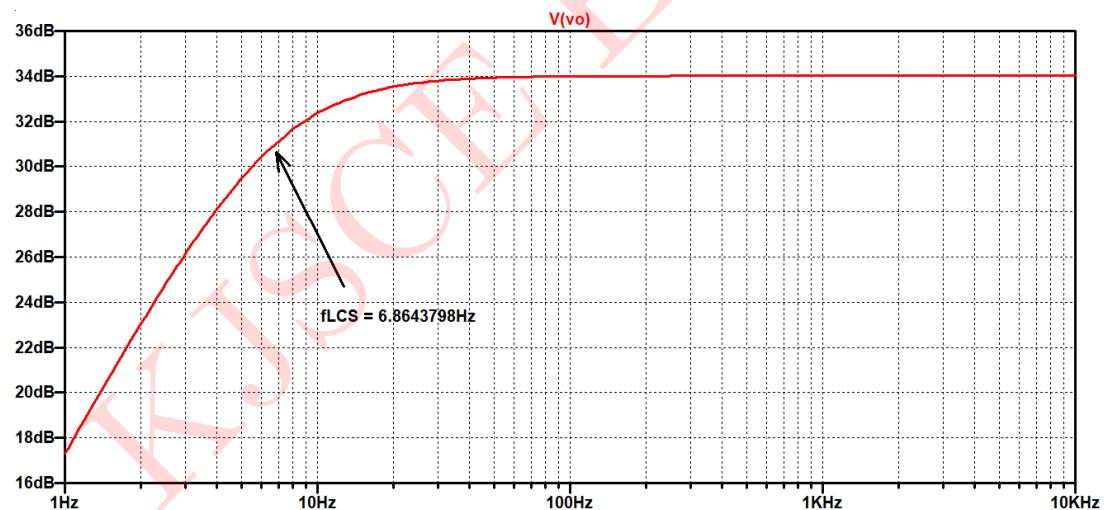


Figure 35: Low Frequency Response for  $C_S$

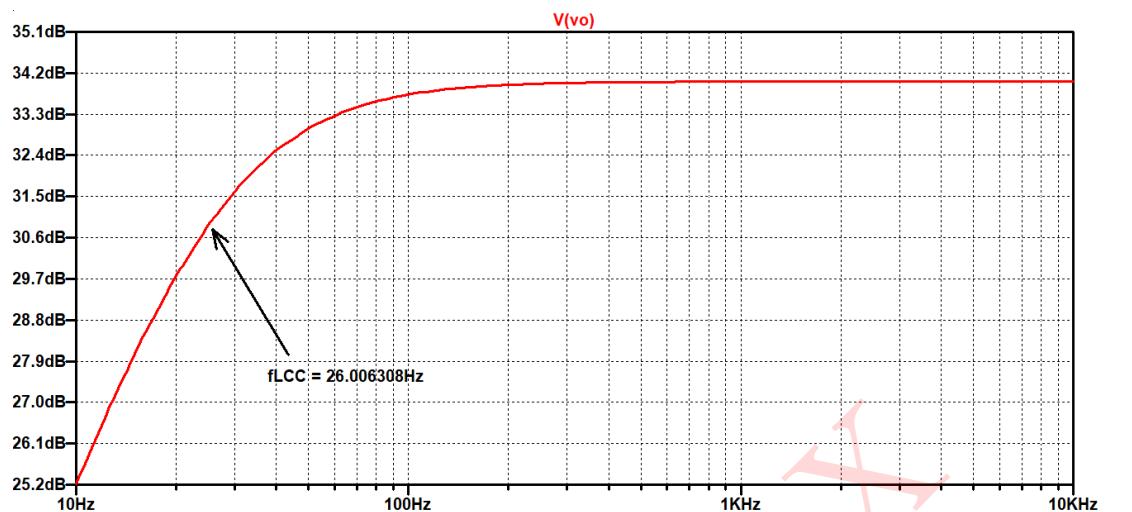


Figure 36: Low Frequency Response for  $C_C$

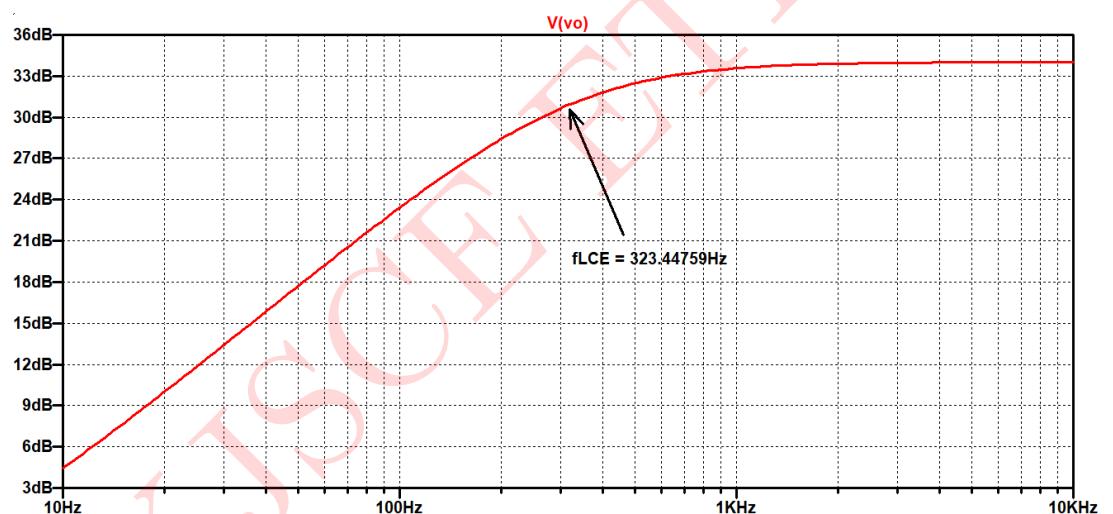


Figure 37: Low Frequency Response for  $C_E$

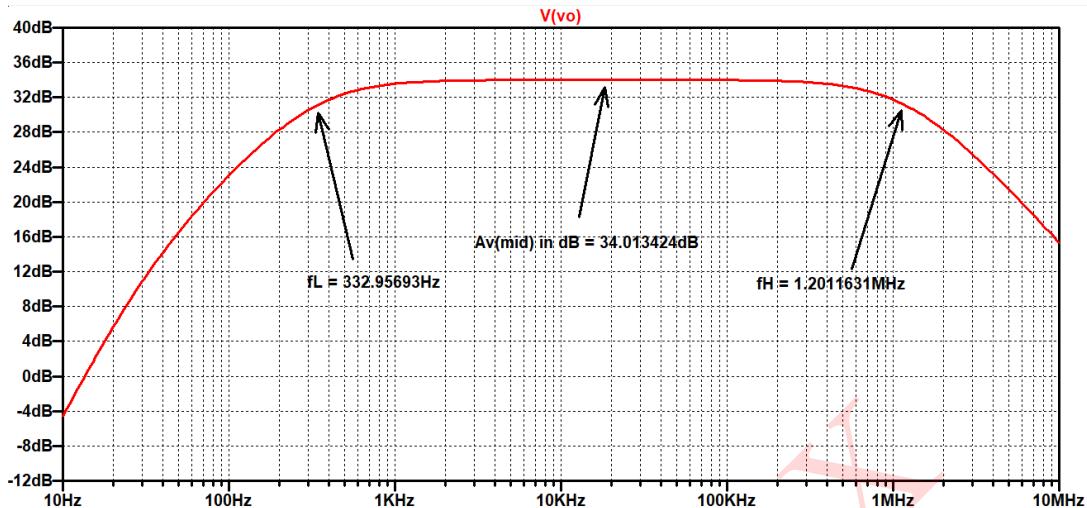


Figure 38: Low Frequency Response for the Circuit

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{CQ}$	1.571 mA	1.5923 mA
$V_{CEQ}$	10.544 V	10.4141 V
Lower cut-off frequency due to $C_S$	6.741 Hz	6.8643 Hz
Lower cut-off frequency due to $C_C$	25.67 Hz	26.0063 Hz
Lower cut-off frequency due to $C_E$	321.785 Hz	323.4475 Hz
Overall cut-off frequency $f_L$	321.785 Hz	332.9569 Hz
Overall cut-off frequency $f_H$	1.1329 MHz	1.2011 MHz
Midband voltage gain $A_{V(mid)}$ in dB	33.8789 dB	34.0134 dB

Table 3: Numerical 3

\*\*\*\*\*